
MIPS Single Cycle Project

 

Designed by Yaniv Cohen Zagouri

Github



Schematic 1: MIPS shematic

Example of MIPS single cycle processus

This is the full code that was uploaded to the Instruction Memory:


```
addi $t0, $zero, 0
                             ; $t0 = 0
                                                 ; counter
    addi $t1, $zero, 5
                             $$t1 = 5
                                                 ; limit
loop:
   slt $t2, $t0, $t1 ; $t2 = ($t0 \ $\frac{1}{2} \); if $t2 == 0, exit loop
                             ; $t2 = ($t0 < $t1) ? 1 : 0
    addi $t0, $t0, 1
                             ; $t0 = $t0 + 1
         loop
                             ;repeat loop
    j
end:
         $t0, 0($s1)
                             ; store final value of $t0 at address
    SW
in $s1
```

In the next images, we will decode the five different parts of the cycle using Instruction 2 as an example:


addi \$t1, \$zero, 5



Waveform1: Fetch and Decode part

 

Waveform2: Execute, Memory Access and Write Back

 

Waveform3: Value of important register and M(\$S1) during tb

1. Fetch:

- → The **PC** (Program Counter) reads the instruction from address x"00000004" in the instruction memory.
- → It is also incremented by 4 (since each instruction is 4 bytes) to point to the next instruction at address x"00000008".

2. Instruction Decode:

- → The instruction (x"20090005") is broken down and sent to different components:
 - Reg_File (for reading registers),
 - Control Unit (to understand the instruction),
 - The **control unit** takes the **opcode** (x"08"), which tells the processor what operation to perform (in this case, addi).

3. Execute:

- → The ALU performs the operation given by the ALU Control. Here:
 - A = 0 (the value in register \$zero), B = 5 (the immediate value), Alu Ctrl= 2 (which means "add")
 - Alu Rslt= 5

4. Memory Access:

→ This instruction (addi) does not read from or write to memory.Instead, it modifies a **register** value.

5. Write Back:

→ We store the result 5 into the **Register File** at address x"09", which is register \$t1.Now \$t1 = 5

In a single-cycle processor, all these steps happen in **one single clock cycle**. That means even simple instructions (like add) and more complex ones (like load) take the **same amount of time**.